


Register Level Transfer (Ch 8 Hayes)

The ALU "Arithmetic Logic Unit":

- Arithmetic and Logic Operations:**

$F = A \text{ OP } B$ A, B, F are 4 BIT Variables

 $F_0 = (M + CN) \text{ XOR } !(A_0 + B_0 S_0 + B_0 !S_0) \text{ XOR } !(A_0 !B_0 S_2 + A_0 B_0 S_3)$



Examples of Different Operations in ALU

- **Need to perform $F=A \text{ PLUS } B$**

$M=0$ (Arithmetic)

$!C_n=1$ (no carry in)

$S_3S_2S_1S_0=1001$

- **need $F= A \text{ XOR } B$**

$M = 1$ Logic

$S_3S_2S_1S_0=0110$

- **Need $F=0$**

$M=1$ Logic

$S_3S_2S_1S_0=0011$

Data and Control

Control:


Sets control signals for Data Path unit to operate on input.

Consists of : Counters, FSM, Shift registers


Data Path:

to perform operations

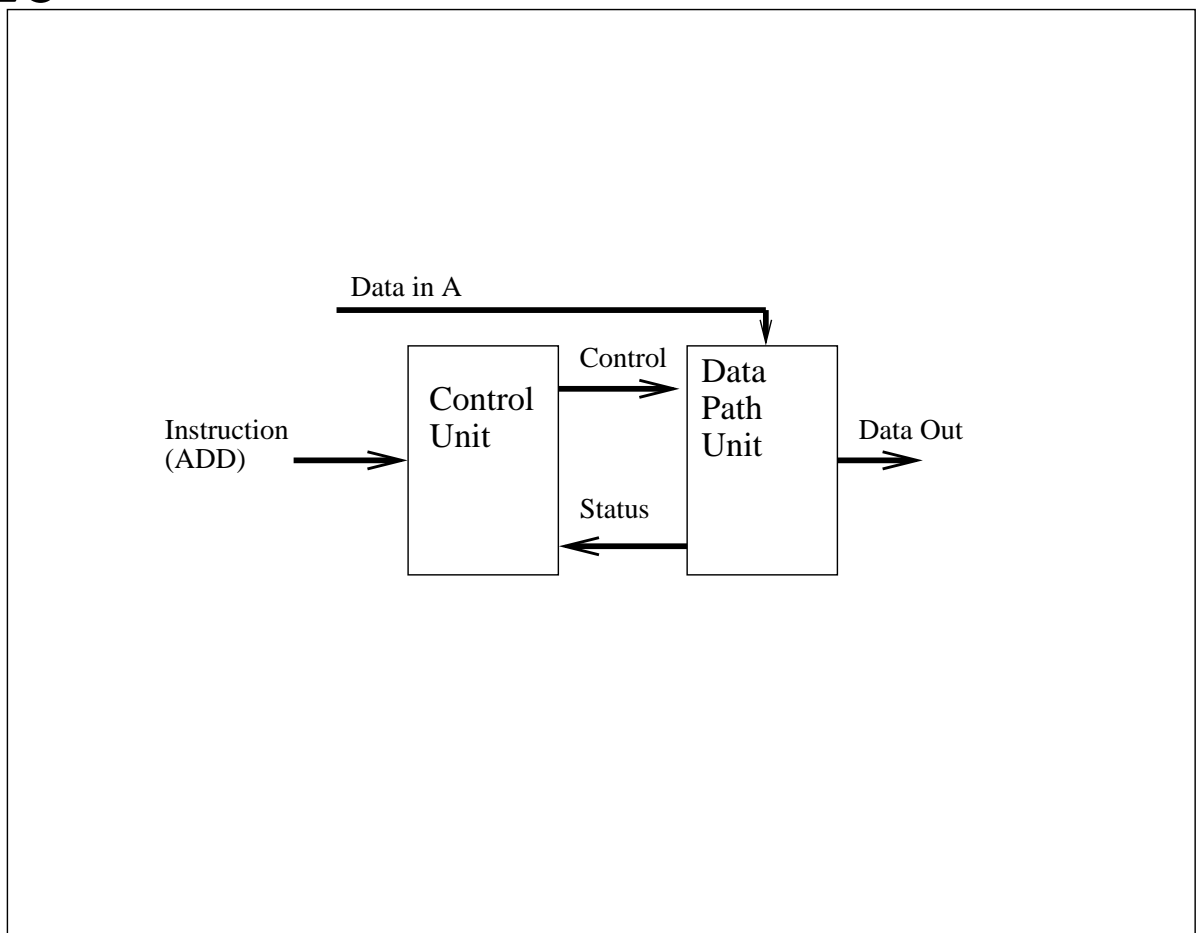consists of: Logic gates, Multiplexers, decoder, ALU



Small Processor

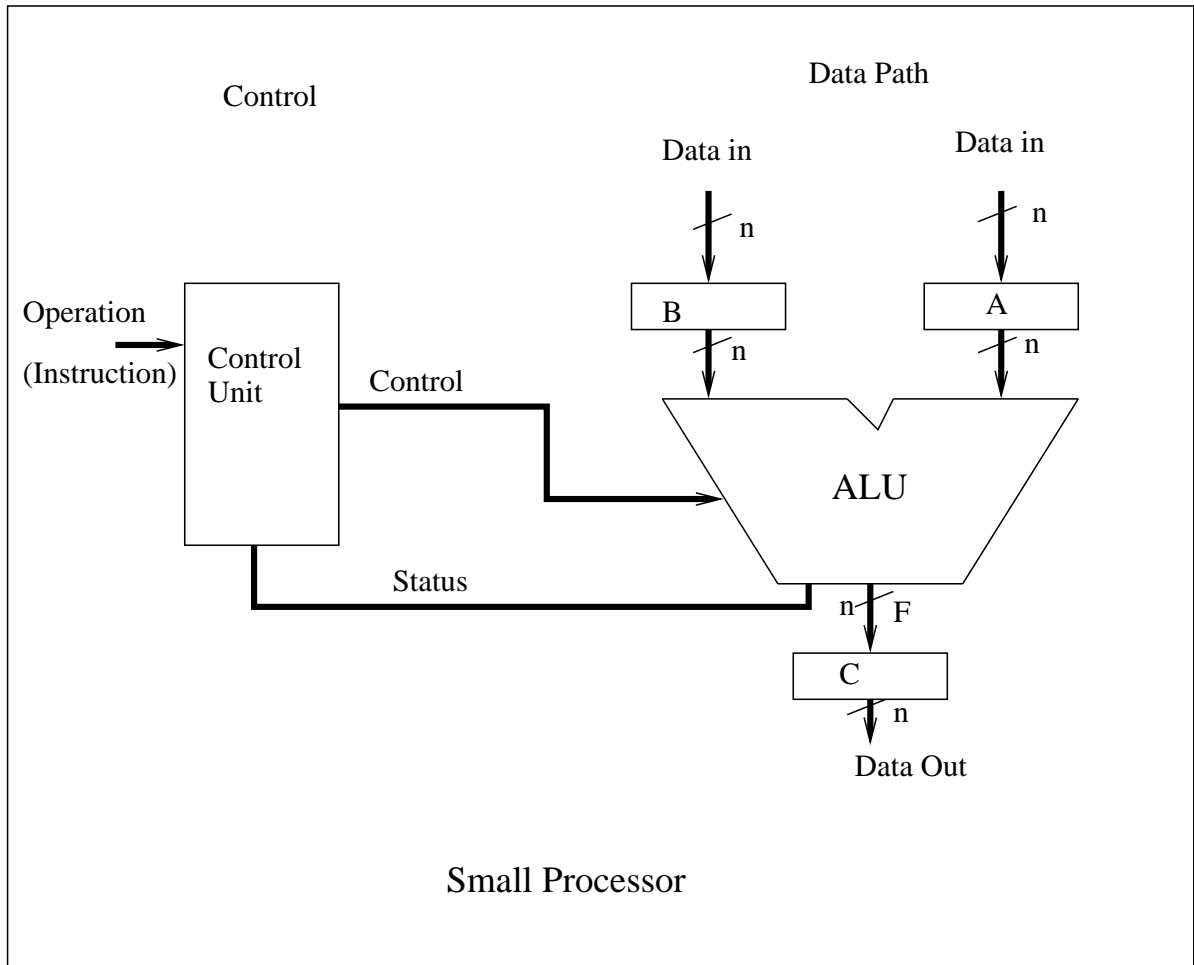

Example:

Instruction: $C = A - B$

Steps:

Control unit sets values of $S_3S_2S_1S_0$, M , C_n for Subtraction

Next cycle it Store F in Register C (Load)

Check Overflow (status) ©N. Mekhiel

Structure of Data Path Units


Inside the CPU to perform Arithmetic and Logic Operations

It operates on Data stored in Registers as Operands.
The Result is stored in Register.

Need ALU to perform operation

Need Registers to store operands and results

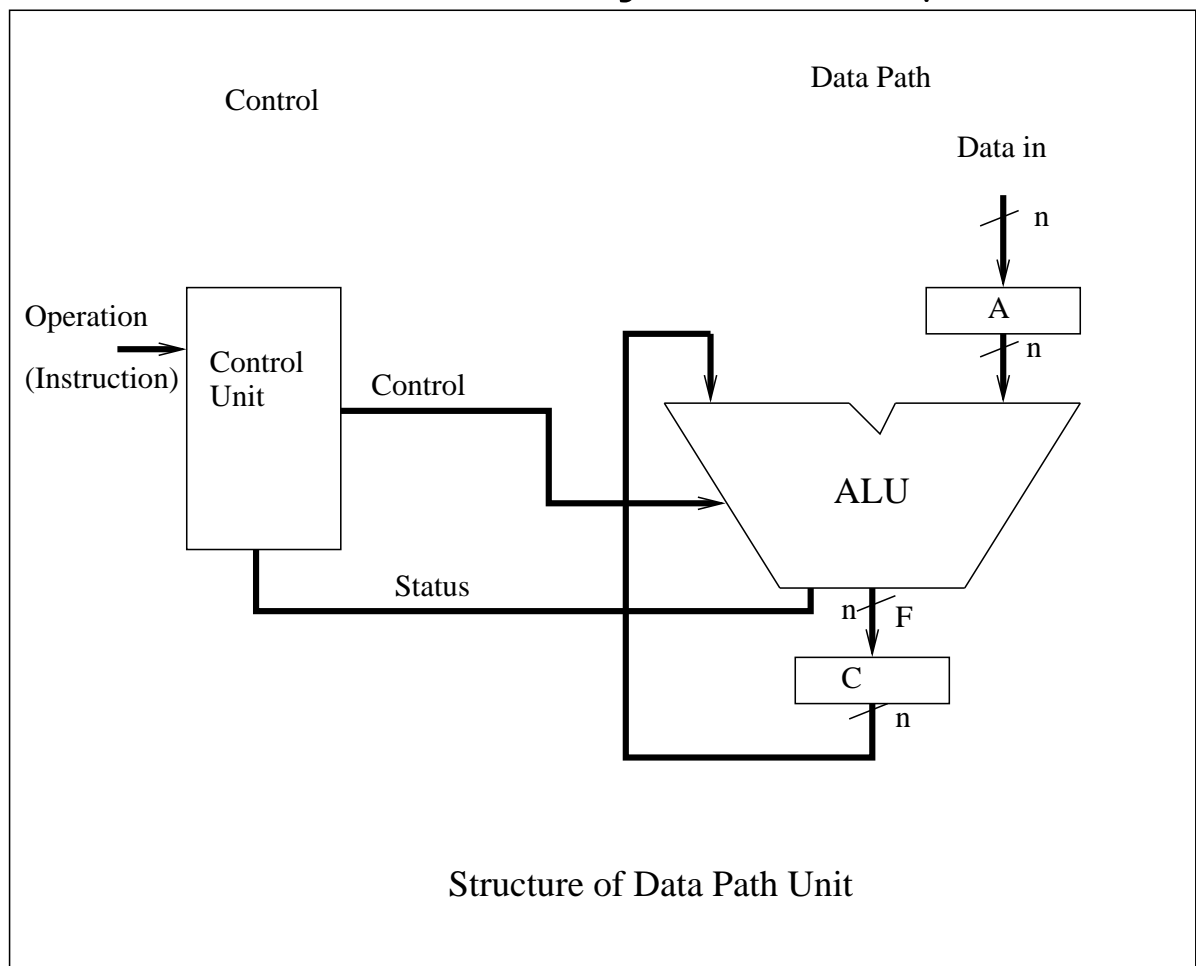Need specific connection (structure) of above components that is defined by the data path.




Operation: ADD two numbers from input1 (X1, X2)

- CLR B
- LDA X1 (A=X1)
- ADD; ALU OUT=X1+0
- LDB X2; A=X2
- ADD; ALU OUT= X1 + X2
- LDB ; B= X1+X2

©N. Mekhiel

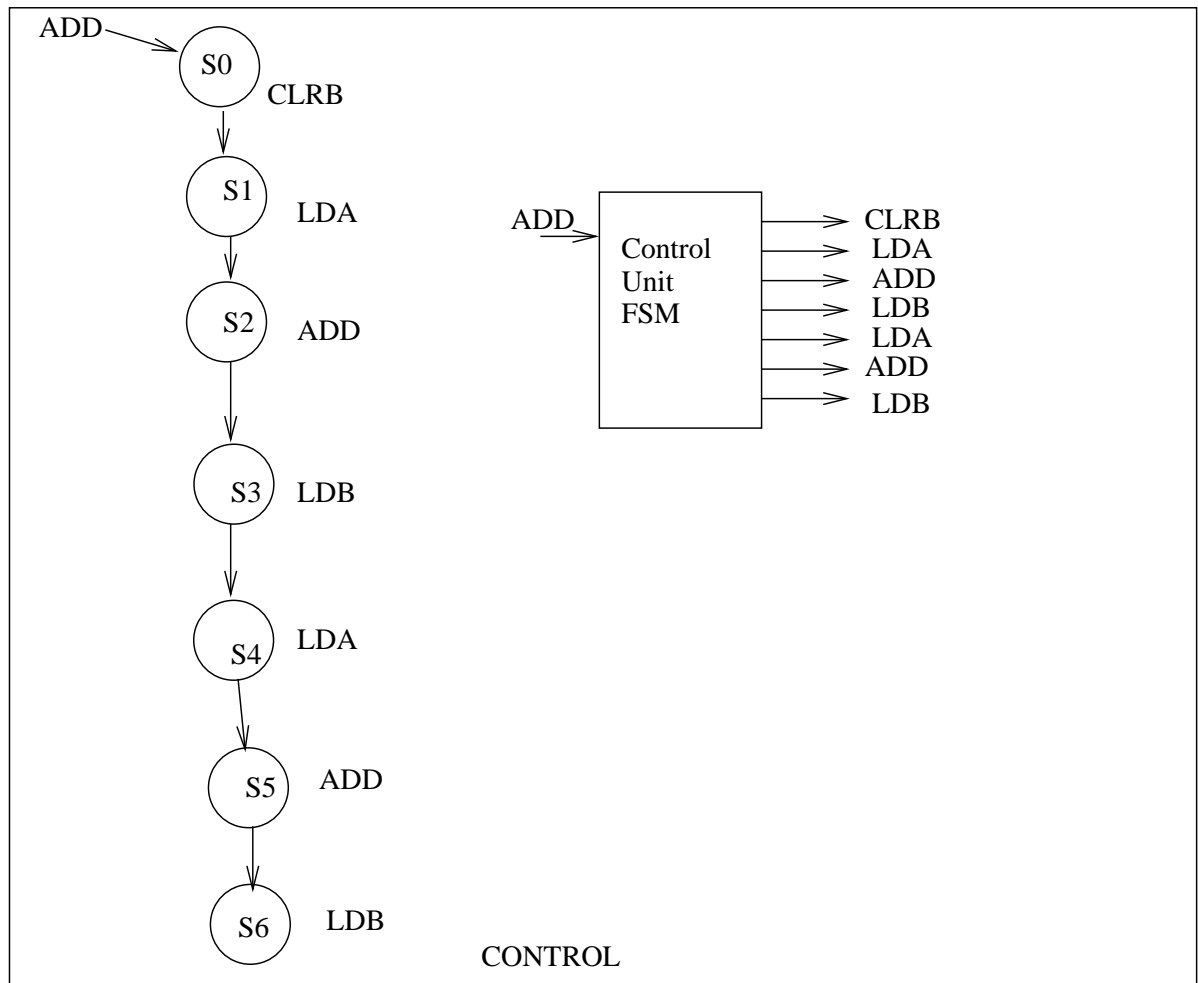Control: ADD two numbers from input1 (X1, X2)



©N. Mekhiel

Improving Performance of Serial Type of Operations with "Pipelining"

Concept of Pipelining: Overlap operations on time so that multiple operations are done in parallel

Example: CAR Assembly Line with 3 steps:

1-Stage 1: ENGINE


2-Stage 2: Body

3-Stage 3: Interior

CPU Uses pipelining for instructions as:

Each instruction is divided to : FETCH, DE-CODE, EXECUTE, WRITE Stages ©N. Mekhiel

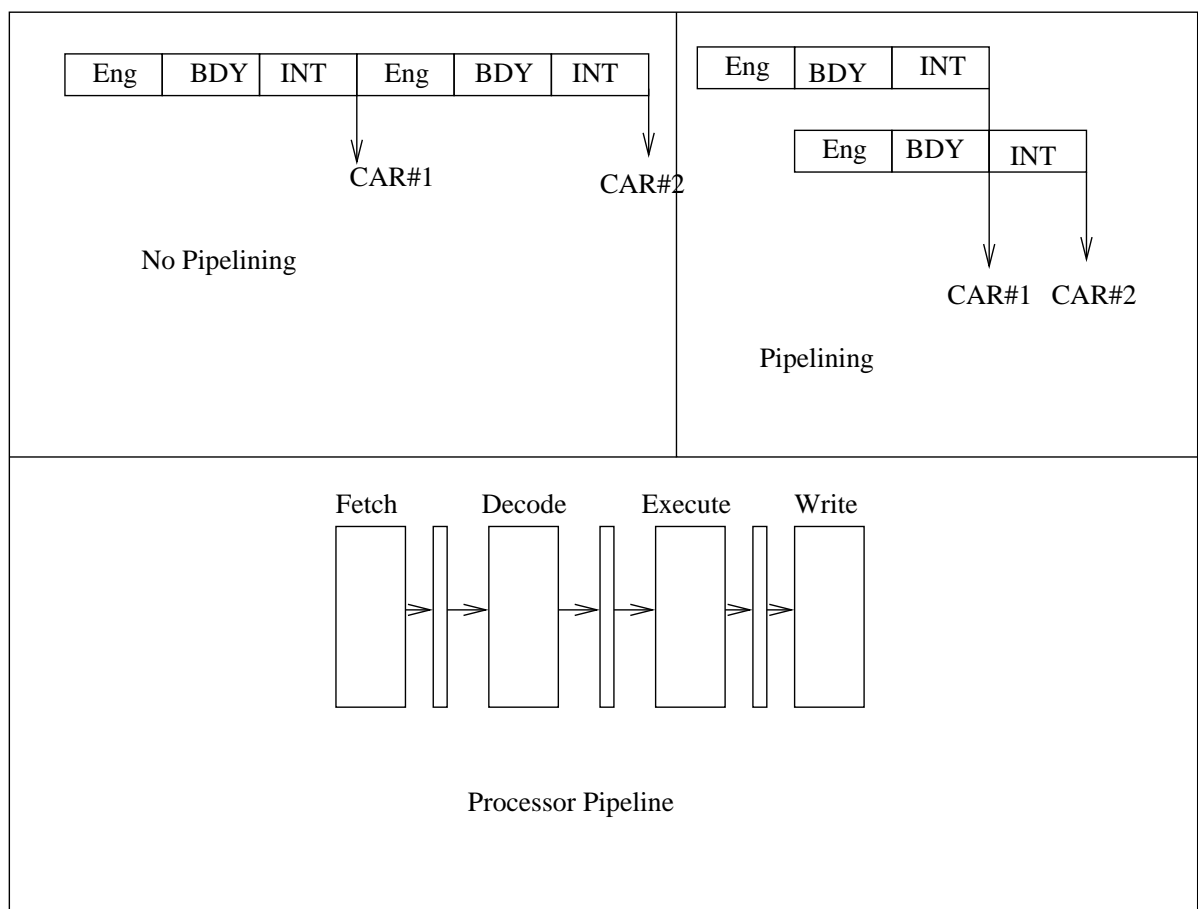Improving Performance of Serial Type of Operations with "Pipelining"




©N. Mekhiel

Scaling

Scaling Down: from larger to smaller

From smaller to larger using BIT SLICE (difficult to scale most functions)

Examples: ADDRER, ALU, SHIFT REGISTER

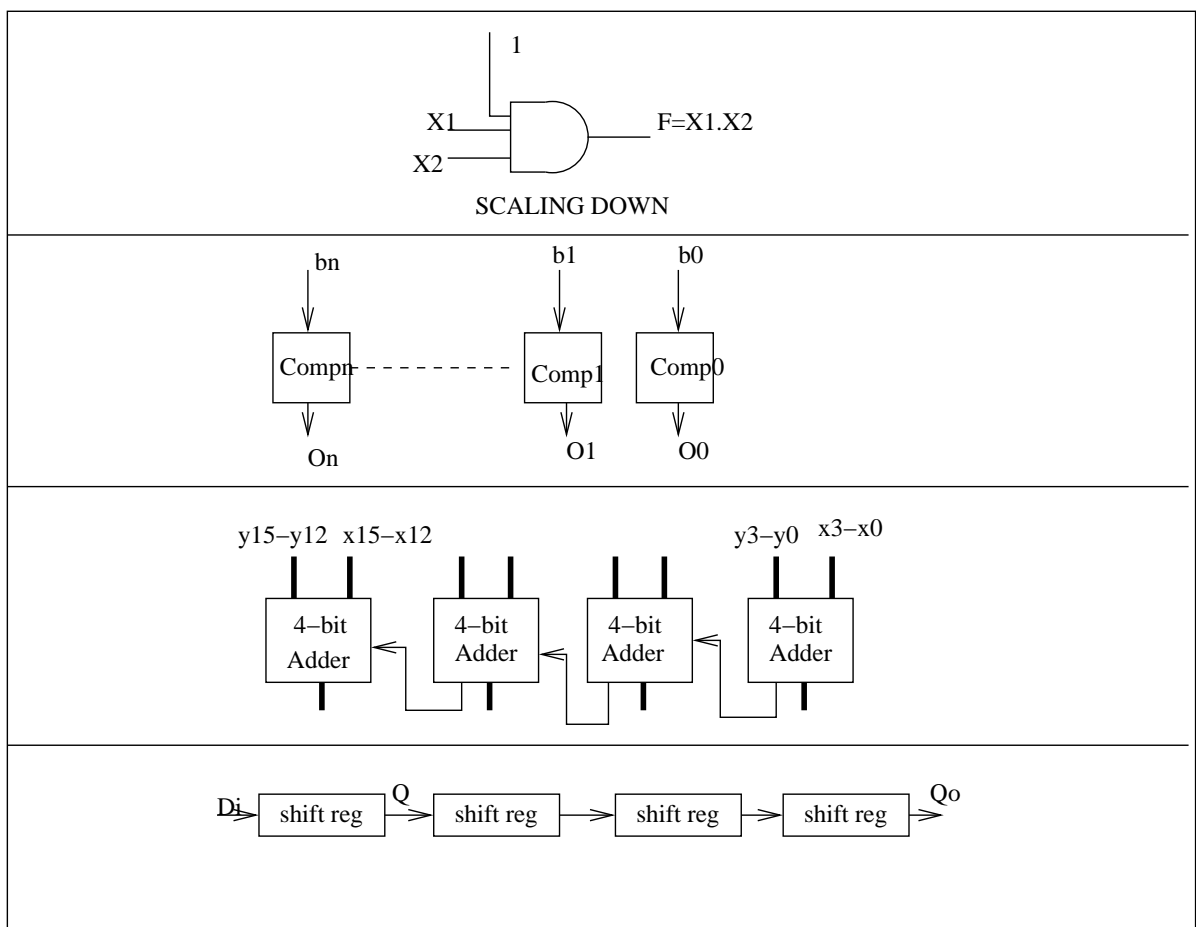

©N. Mekhiel

Control Units "Microprogramming"

Types:

FSM


Microprogramming

One -Hot Method (Shift Register)

Microprogramming Advantages: Easy to change microinstructions with software

Consists of ROM to store that Data required to change Present state to next state (combinational circuit used in FSM).

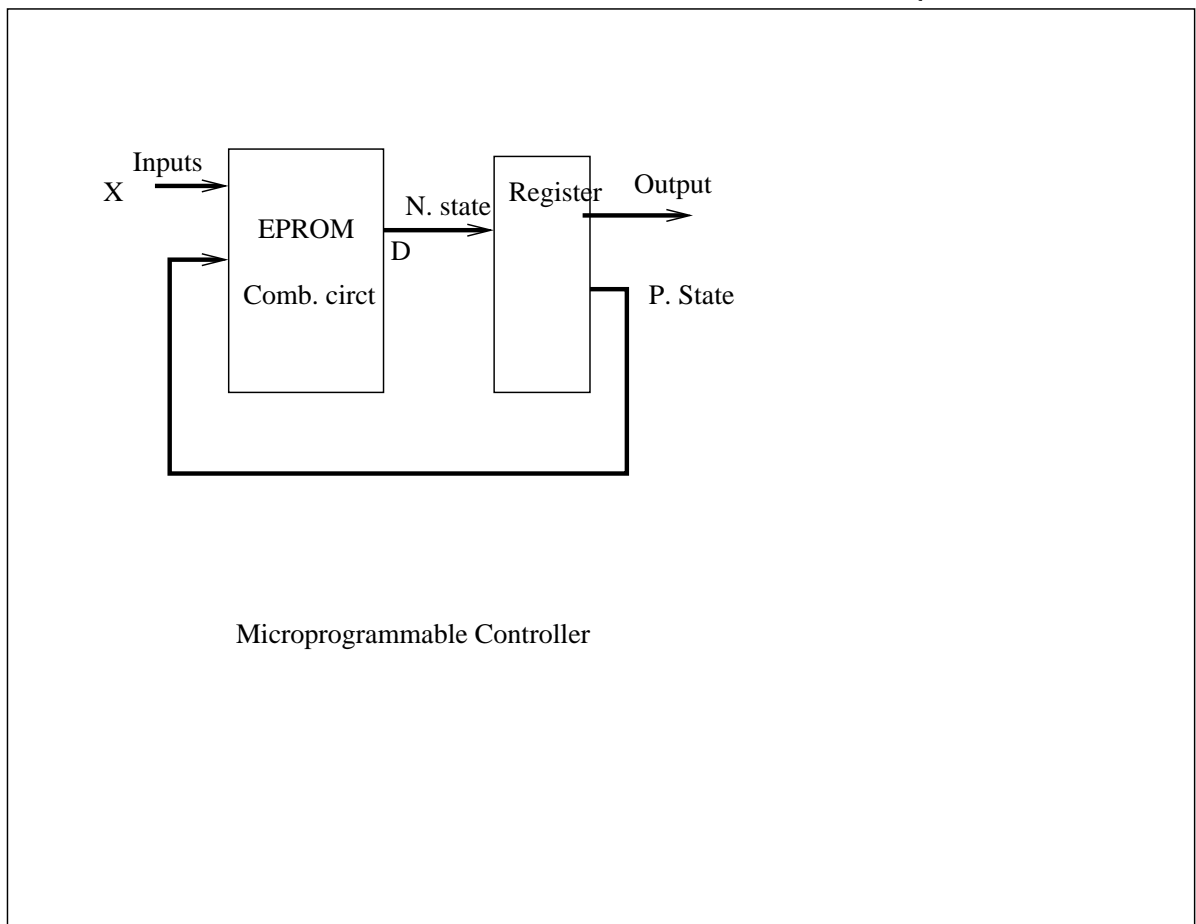Register used to store present state (F-F in FSM)



©N. Mekhiel