


# Chapter 3

3.1. (a)

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) #transistors = 48

3.2.

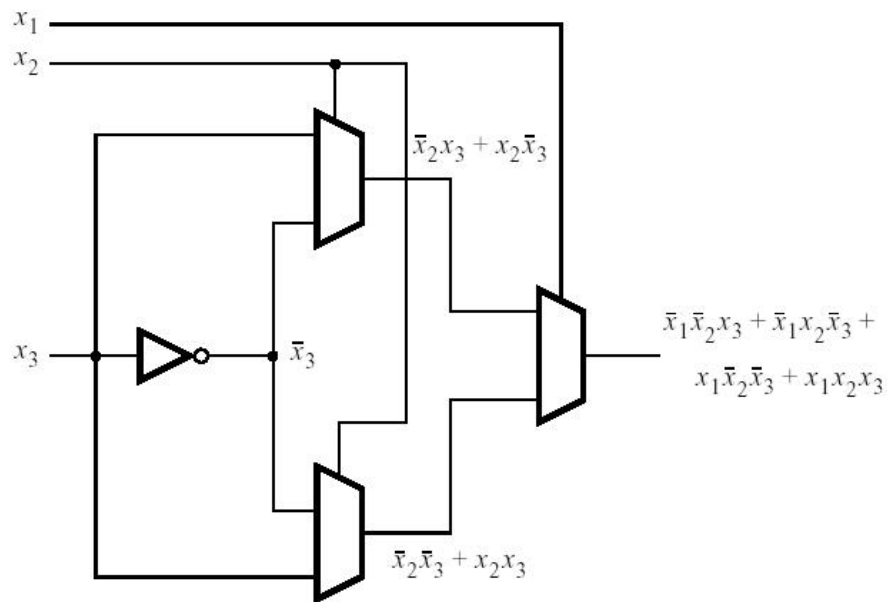

3.3. (a)  $x_1\bar{x}_2\bar{x}_3 + \bar{x}_1x_2\bar{x}_3 + \bar{x}_1\bar{x}_2x_3 + x_1x_2x_3$

(b) #transistors =  $2 \times 8 = 16$

3.4. The number of transistors needed is 16.

3.6. (a)

$x_1$	$x_2$	$x_3$	$f$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

(b) #transistors = 58


3.7. (a)

$x_1$	$x_2$	$x_3$	$x_4$	$f$
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0


$x_1$	$x_2$	$x_3$	$x_4$	$f$
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

(b) #transistors = 28


3.8.

 


3.9.

 


3.11.

 

3.12.

 

3.13.

 

3.25. (a)


$$NM_H = 0.5 \text{ V}$$

$$NM_L = 0.7 \text{ V}$$


(b)  $V_{OL} = 0.8 \text{ V}$

$$NM_L = 0.2 \text{ V}$$


3.36.

 


3.37.

 


3.38.

 


3.39.

 


3.44.

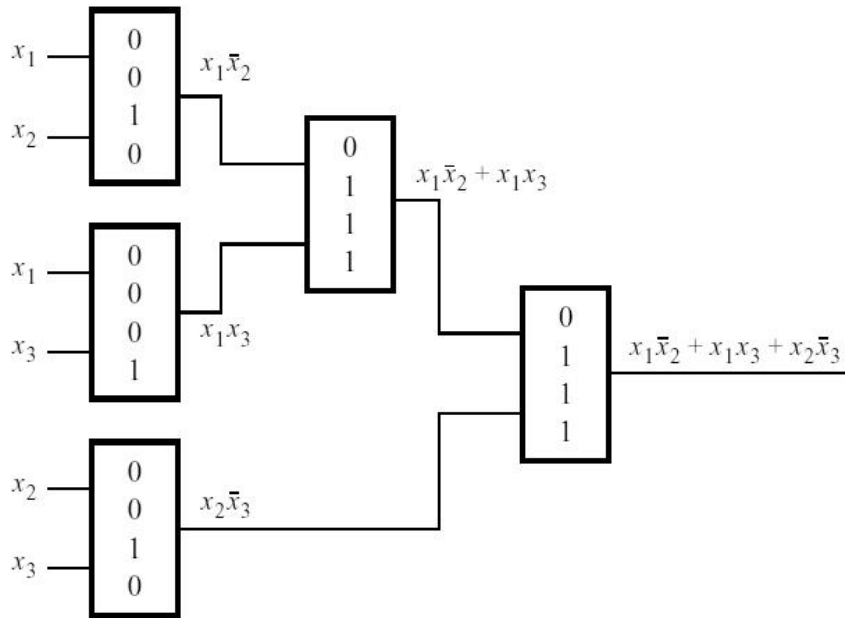


3.45.

 


3.46.

 

3.47.

 


3.49. (a)

 





(b)

 

3.50. (a)

 

(b)

 

```

3.51.      LIBRARY ieee ;
           USE ieee.std_logic_1164.all ;

           ENTITY prob3_51 IS
               PORT ( x1, x2, x3, x4 : IN    STD_LOGIC ;
                     f               : OUT  STD_LOGIC ) ;
           END prob3_51 ;

           ARCHITECTURE LogicFunc OF prob3_51 IS
           BEGIN
               f <= (x2 AND NOT x3 AND NOT x4) OR
                   (NOT x1 AND x2 AND x4) OR
                   (NOT x1 AND x2 AND x3) OR (x1 AND x2 AND x3) ;
           END LogicFunc ;

3.52.      LIBRARY ieee ;
           USE ieee.std_logic_1164.all ;

           ENTITY prob3_52 IS
               PORT ( x1, x2, x3, x4 : IN    STD_LOGIC ;
                     f               : OUT  STD_LOGIC ) ;
           END prob3_52 ;

           ARCHITECTURE LogicFunc OF prob3_52 IS
           BEGIN
               f <= (x1 OR x2 OR NOT x4) AND
                   (NOT x2 OR x3 OR NOT x4) AND
                   (NOT x1 OR x3 OR NOT x4) AND
                   (NOT x1 OR NOT x3 OR NOT x4) ;
           END LogicFunc ;

```